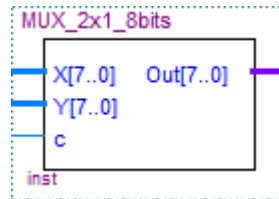


Report


Name: MUX_2x1_8bits

Simulation: 2 to 1 8 bits multiplexer.

Symbol:



Circuit:

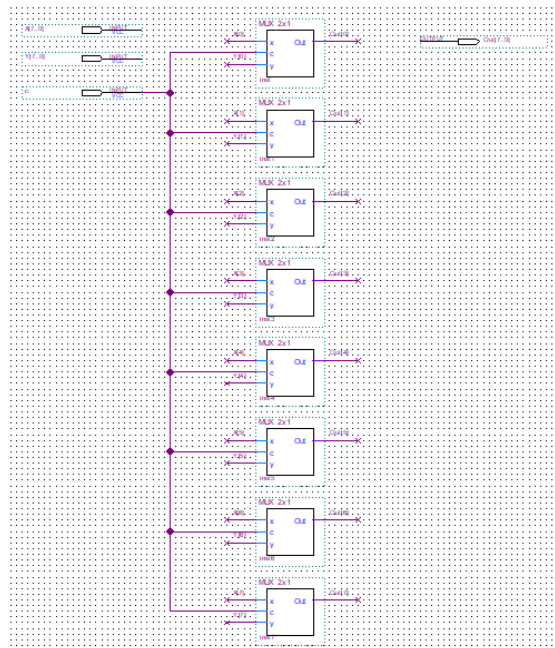

Simulation:

