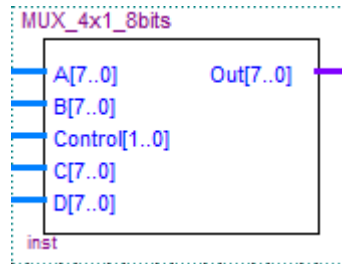


Report


Name: MUX_4x1_8bits

Simulation: 8 bits 4 to 1 multiplexer.

Symbol:



Circuit:

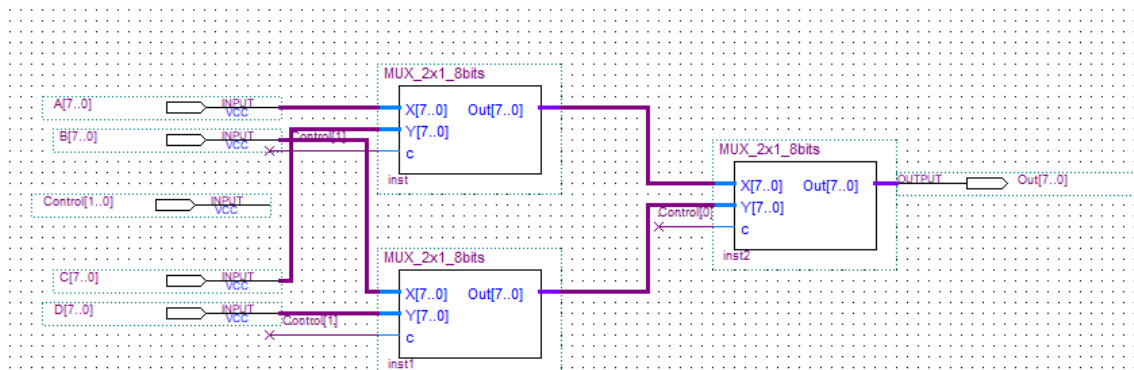

Simulation:

