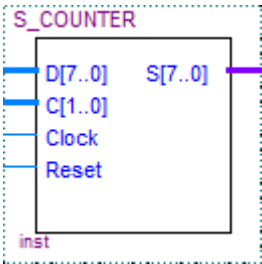


Report


Name: S_COUNTER

Simulation: 8 bits synchronous generic counter. It's up counter, down counter, keep value and set value.

Symbol:



Circuit:

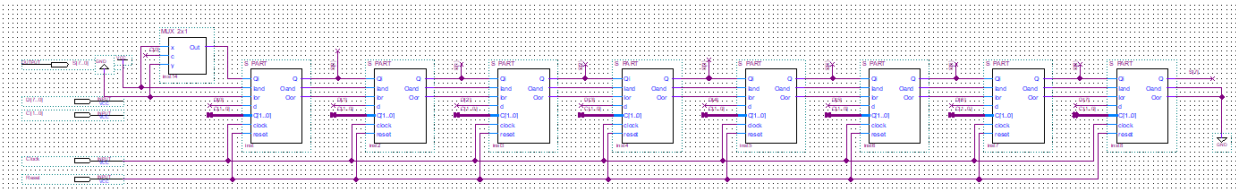

Simulation:

