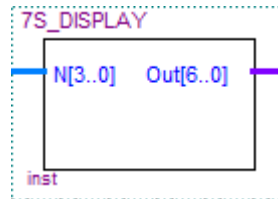


Report


Name: 7S_DISPLAY

Description: 7 segments display.

Symbol:



Circuit:

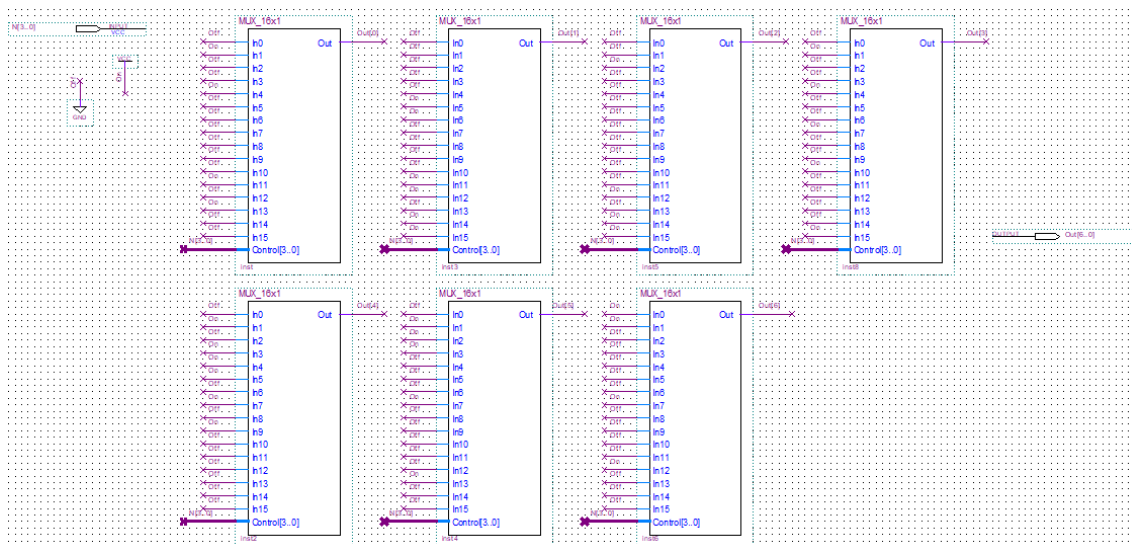

Simulation: QUARTUS III University Program doesn't run with a number at name's begin. However, it's working as expected.