
## Report


Name: CONTROL

**Description:** this circuit is the control unit of neander. It gives signals when it's necessary, controlling all the processor.

## Symbol:

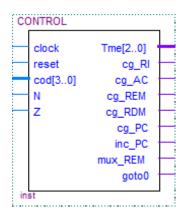



## Circuit:

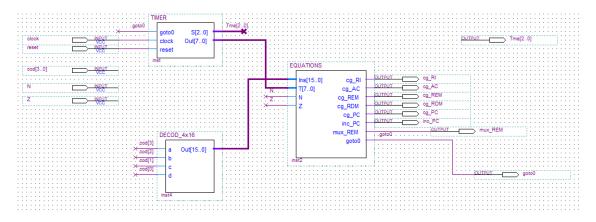


## Simulation:

• NOP (cod = 0x0000):

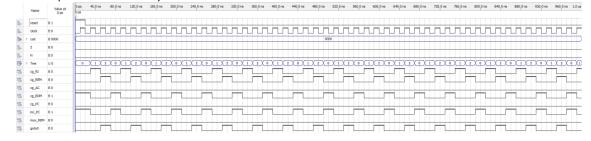


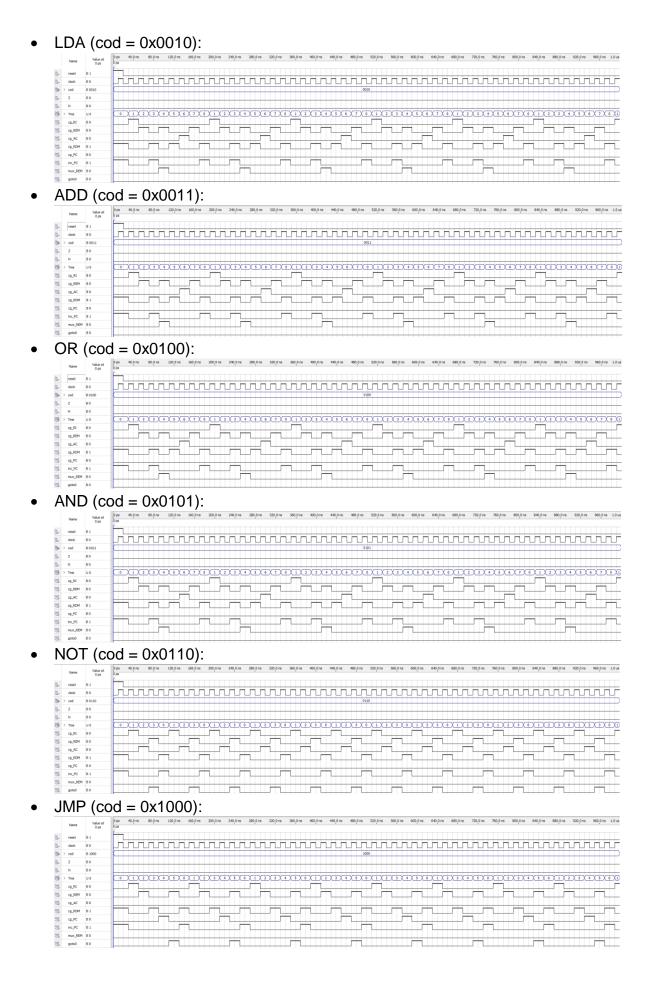

• JN (cod = 0x1001):

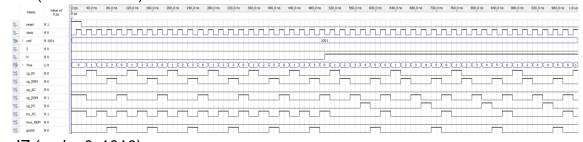

• JZ (cod = 0x1010):

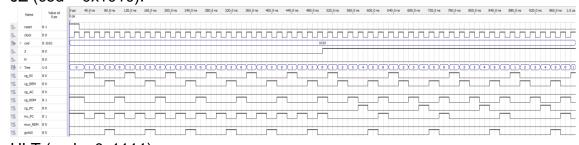

HLT (cod = 0x1111):

